

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE & ENGINEERING**

**DEPARTMENT OF PHYSICS**

**SUPPLEMENTARY EXAMINATION 2013**

**TITLE OF PAPER : ELECTRONICS I**

**COURSE NUMBER : P311**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE  
SHOWN IN THE RIGHT-HAND MARGIN.**

**THIS PAPER HAS 9 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE  
INVIGILATOR.**

### QUESTION 1

- (a) Explain how you would measure the characteristics of an n-p-n transistor when it is connected in the CE configuration. Use a circuit diagram for illustration. (2 marks)
- (b) Sketch the output characteristics of an n-p-n transistor and show the cut-off and active regions. (4 marks)
- (c) The transistor used in the circuit shown in Fig. 1 has an a.c. current gain,  $h_{fe} = 200$  and input resistance,  $h_{ie} = 7 \text{ k}\Omega$ . The reverse saturation current is negligible. The base-emitter voltage,  $V_{BE} = 0.7 \text{ V}$ . Calculate the collector current and the collector-emitter voltage. (11 marks)
- (d) (i) Draw a simplified small-signal model of the circuit shown in Fig. 1 and label it. Why is the output resistance of the transistor usually neglected in the circuit? (4 marks)
- (ii) Derive an expression for the voltage gain of this circuit. (2 marks)
- (iii) Calculate the voltage gain of the circuit using the data given in Q.1(c) above. (2 marks)

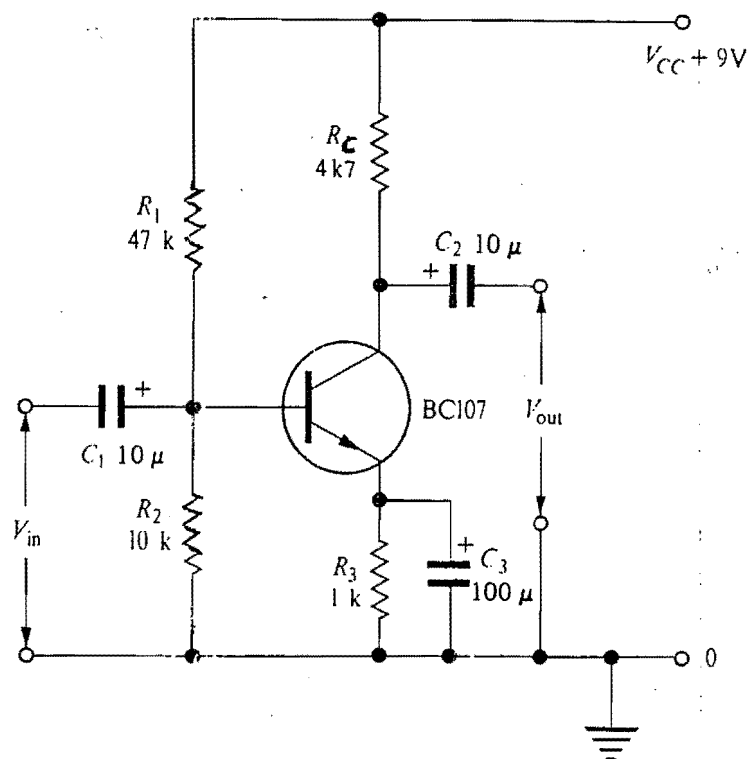


Fig. 1

**QUESTION 2**

- (a) Write down the equation for a *p-n* junction diode which describes the relationship between the (*p-n*junction) diode current and the diode voltage. Explain what each symbol stands for. (6 marks)
- (b) Sketch the current-voltage characteristics of diodes made of silicon and germanium and show the turn-on voltage for each diode. (2 marks)
- (c) The characteristic shown in Fig. 2 represents the silicon diode in Fig. 3.
- (i) Use Fig. 2 and Fig. 3 to estimate the diode current and diode voltage. [Hint: Utilise the enlarged Fig. 2 given on page 7]. (6 marks)
- (ii) Calculate the new value of  $R$  when  $V_S$  is reduced from 1 V to 0.9 V. Assume that the diode current remains at the value calculated in (i). (4 marks)
- (d) A 4.7 V, 0.5 W Zener diode is used in the simplified regulator circuit shown in Fig. 4. The input voltage,  $V_{in}$  varies from 4 V to 7 V and the load current is 10 mA. Estimate the series resistance  $R_S$  and comment on the value obtained with respect to the operation of the regulator. (7 marks)

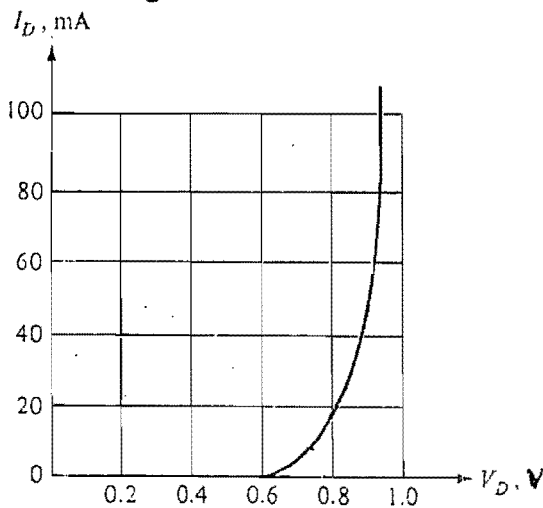


Fig. 2

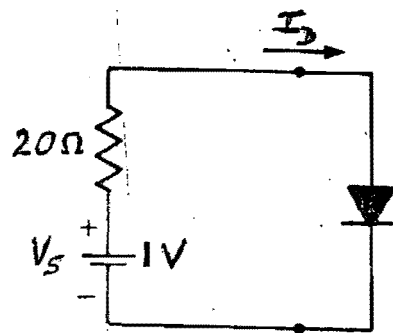


Fig. 3

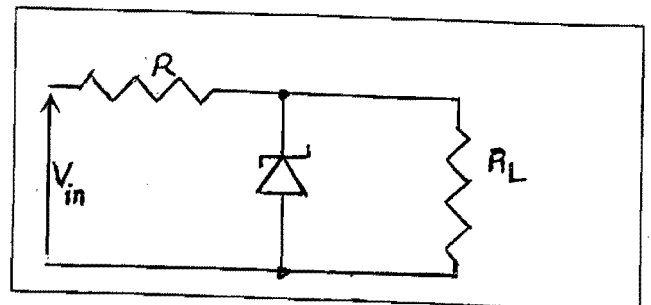


Fig. 4

### QUESTION 3

- (a) Draw the circuit diagram of a differential amplifier and label it. (3 marks)
- (b) The equations below provide information about the relationship between the currents and voltages associated with a differential amplifier.

$$i_{d1} \approx \frac{g_m}{2} [v_{i1} - v_{i2}]$$

$$i_{d2} \approx \frac{g_m}{2} [v_{i2} - v_{i1}]$$

where  $v_{i1}$  and  $v_{i2}$  are the input voltages to the amplifiers consisting of transistors  $T_1$  and  $T_2$  respectively;  
 $i_{d1}$  and  $i_{d2}$  are the drain currents;  
 $g_m$  is the mutual conductance;  
 $R$  is the source resistance.

Use the above equations to show that the output voltages of the differential amplifier are equal in magnitude but out of phase by  $180^\circ$ . (11 marks)

- (c) (i) Draw the circuit diagram of a source follower. (3 marks)
- (ii) Explain why the circuit is called a source follower. (2 marks)
- (iii) Show that the output resistance of a source follower is inversely proportional to the mutual conductance. (6 marks)

**QUESTION 4**

(a) Define the following terms:

(i) *mutual conductance,  $g_m$*  and (2 marks)

(ii) *drain resistance,  $r_d$*  of a JFET. (2 marks)

(b) The equation below shows the relationship between the drain current,  $I_D$  and the gate-source voltage,  $V_{GS}$  for a junction gate field effect transistor (JUGFET). Use this equation to sketch the mutual characteristic curve when  $V_p = -2$  V and  $I_{DSS} = 8$  mA. (4 marks)

$$\left(\frac{I_D}{I_{DSS}}\right)^{1/2} + \frac{V_{GS}}{V_P} = 1$$

(c) An n-channel JFET is used to build an automatic-biasing common-source amplifier. Sketch the circuit diagram of this type of amplifier and label it. (2 marks)

(d) With the aid of a small signal equivalent circuit, derive an expression for the voltage gain of the amplifier described in Q.4(c) above. (7 marks)

(e) The JFET characteristics shown in Fig. 5 are based on the JFET utilised in Fig. 6. The supply voltage,  $V_{DD} = 25$  V, and it is desired that  $V_{DS} = 12.5$  V and  $I_D = 2.5$  mA at the operating point. Find  $R_D$  and  $R_S$ . Use the enlarged Fig. 5 given on page 8 to find  $R_D$ . (8 marks)

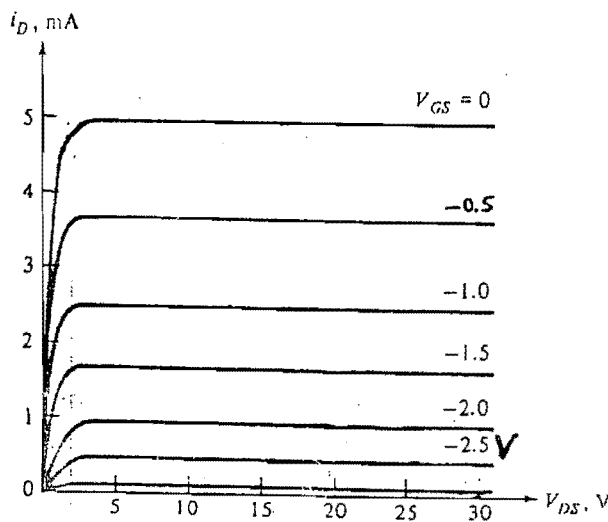


Fig. 5

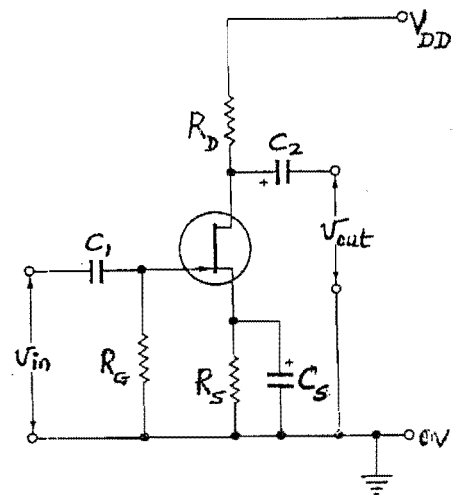



Fig. 6

### QUESTION 5

- (a) What is meant by the following terms:
- (i) *intrinsic semiconductor?* (2 marks)
  - (ii) *valence band?* (2 marks)
- (b) Sketch a two-dimensional crystal structure of silicon that has been doped with phosphorous. Describe the effect of the dopant on the resistivity of the material. (5 marks)
- (c) Sketch the energy-band diagrams for both intrinsic and p-type silicon. Label the diagrams and interpret the meaning of each diagram. (10 marks)
- (d) A germanium diode is operated at a junction temperature of 27°C. For a forward current of 10 mA,  $V_D$  is found to be 0.3 V.
- (i) Find the reverse saturation current. (2 marks)
  - (ii) If  $V_D = 0.4$  V, find the forward current. (4 marks)

**PLEASE SUBMIT THIS PAGE TOGETHER WITH YOUR ANSWER BOOK**


**STUDENT'S EXAMINATION NUMBER:.....**

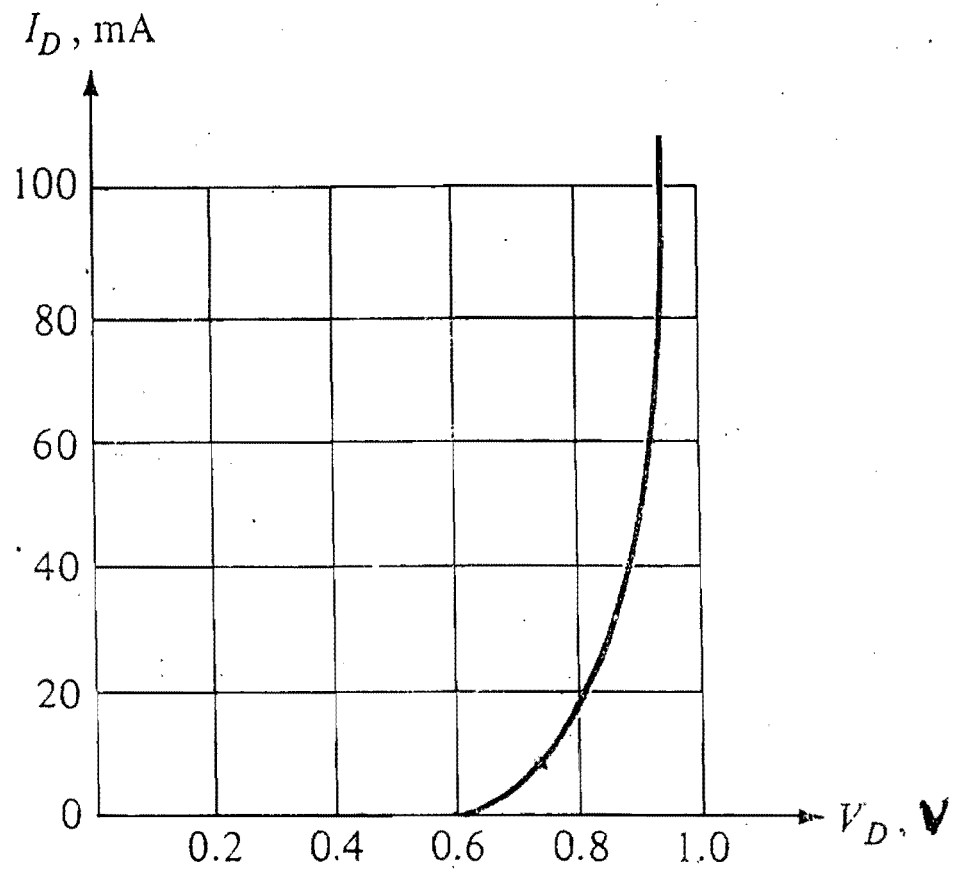

**Fig. 2 (enlarged)**

**PLEASE SUBMIT THIS PAGE TOGETHER WITH YOUR ANSWER BOOK**

**STUDENT'S EXAMINATION NUMBER:.....**

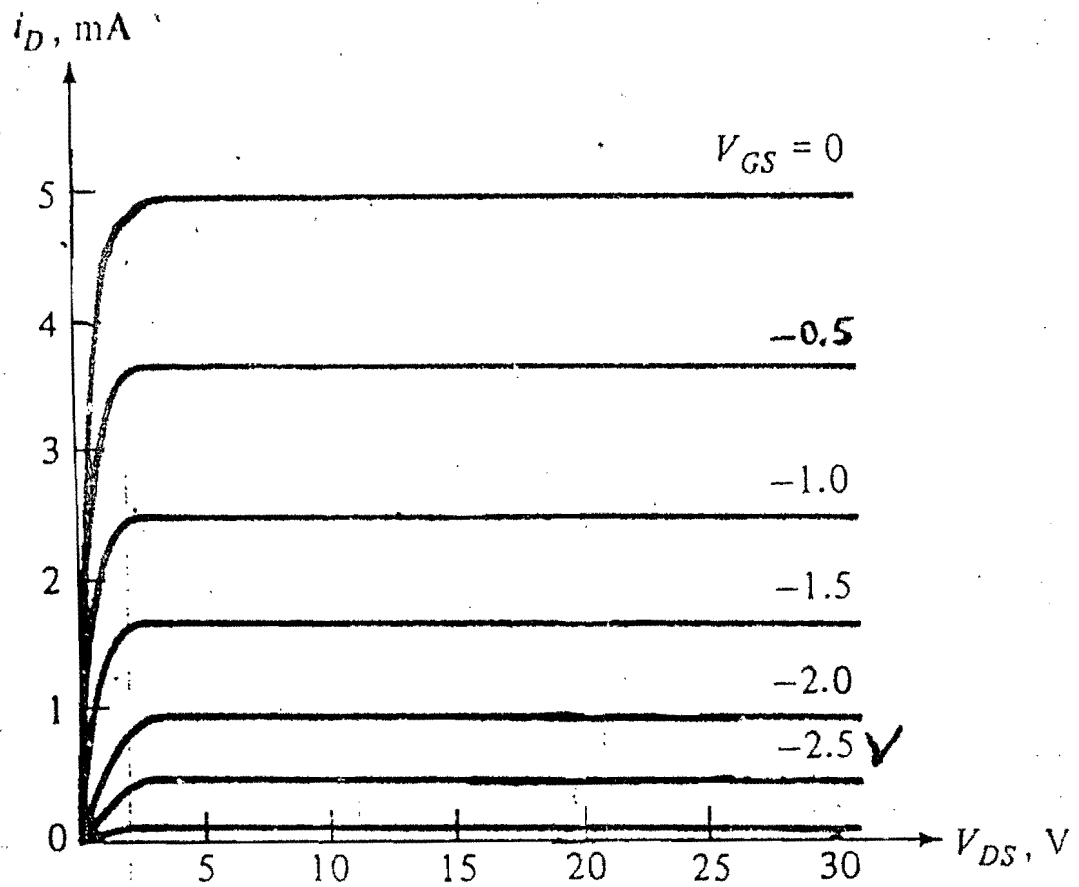

**Fig. 5 (enlarged)**



## PHYSICAL CONSTANTS

Boltzmann constant,  $k$        $= 1.38 \times 10^{-23} \text{ J.K}^{-1}$   
Electronic charge,  $e$        $= 1.6 \times 10^{-19} \text{ C}$