

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE & ENGINEERING**

**DEPARTMENT OF PHYSICS**

**MAIN EXAMINATION : 2012/2013**

**TITLE OF PAPER : ELECTRONICS II**

**COURSE NUMBER : P312**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.**

**THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.**

### **QUESTION 1**

- (a) Define the term 'inverse feedback' with respect to an amplifier. (2 marks)
- (b) Consider a voltage amplifier with an open-loop gain of -500. Negative feedback is applied to the amplifier and the feedback factor is  $5 \times 10^{-3}$ . When the transistor used in this amplifier is replaced, due to ageing, the open-loop gain of the amplifier falls by 20%. What will be the percentage change in closed-loop gain as a result of the decrease in the open-loop gain. (10 marks)
- (c) (i) Sketch the circuit of a phase-shift oscillator that utilises a Darlington pair, resistors and capacitors and explain how it works. (7 marks)
- (ii) The attenuation coefficient of the RC ladder network of a phase shift oscillator is given by

$$B = \frac{1}{[1 - 5\lambda^2] + j[\lambda^3 - 6\lambda]}$$

where  $\lambda = (\omega CR)^{-1}$  and the other symbols have their usual meanings.

Show that the frequency of oscillation of the oscillator is given by

$$f_0 = \frac{1}{2\pi\sqrt{6RC}} \quad (4 \text{ marks})$$

- (iii) Find the numerical value of the attenuation coefficient at the frequency of oscillation. (2 marks)

**QUESTION 2**

(a) With reference to the circuit shown in Fig. 1, calculate the output voltage when  $R_1 = R_2 = R_3 = 10\text{k}\Omega$ ,  $R_4 = 100\text{k}\Omega$ ,  $V_1 = 0.1\text{ V}$ ,  $V_2 = 0.5\text{ V}$  and  $V_3 = 0.25\text{ V}$ . (4 marks)

(b) Calculate  $v_{out}$  as a function of time for an op-amp differentiator, given that  $v_{in} = A\sin \omega t$ , where  $A = 500\text{ mV}$ ,  $\omega = 100\text{ rads}^{-1}$ ,  $C_{in} = 0.1\text{ }\mu\text{F}$  and  $R_f = 200\text{ k}\Omega$ . (6 marks)

Sketch  $v_{in}$  and  $v_{out}$  as a function of time. Label the graphs fully. (5 marks)

(c) (i) Sketch the circuit diagram of a logarithmic amplifier which utilises a pn diode. (2 marks)

(ii) Derive an expression to show that the output voltage,  $V_{out}$  of a logarithmic amplifier is proportional to the logarithm of the input voltage,  $V_{in}$  as follows:

$$V_{out} = -\eta V_T \ln\left(\frac{V_{in}}{I_S R}\right)$$

where the symbols have their usual meanings. (8 marks)

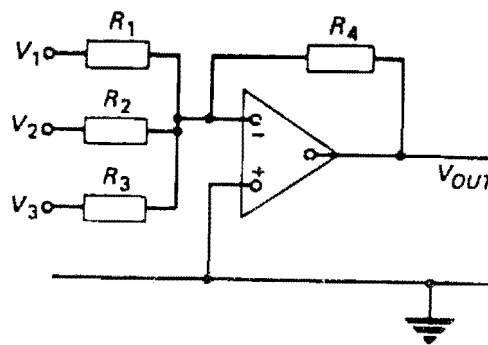


Fig. 1

**QUESTION 3**

- (a) Show that the magnitude of the transfer function of the band-reject filter shown in Fig. 2 is given by the following relationship:

$$|H(s)| = \frac{1}{\sqrt{1 + \left[ \frac{\omega L}{R} - \frac{1}{\omega RC} \right]^2}} \quad (6 \text{ marks})$$

- (b) Given the values of the components shown in Fig. 2, calculate the following:

- (i) the resonant frequency,  $f_0$  of the filter; (3 marks)
- (ii) the quality factor,  $Q_s$ ; (3 marks)
- (iii) the cut-off frequencies,  $f_1$  and  $f_2$ . (5 marks)
- (iv) the bandwidth, BW. (2 marks)

- (c) For the high-pass filter shown in Fig. 3,

- (i) Find the cut-off frequency, in hertz. (3 marks)
- (ii) Find the phase angle between  $v_{out}$  and  $v_{in}$ , when  $v_{in}$  has a frequency of 20 kHz. (3 marks)

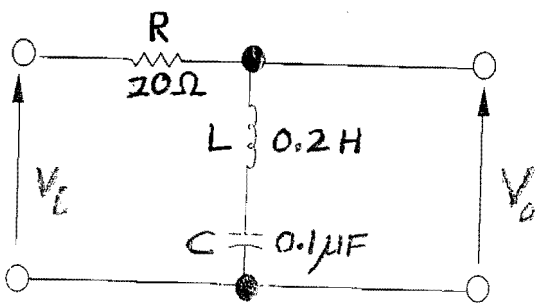


Fig. 2

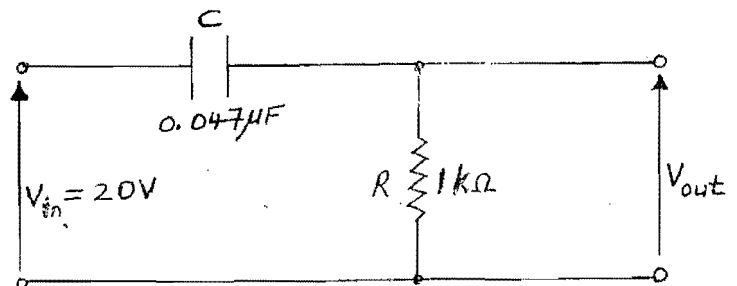


Fig. 3

#### **QUESTION 4**

- (a) (i) Draw the circuit diagram of an emitter follower. (2 marks)
- (ii) With the aid of the small signal equivalent circuit, derive an expression for the voltage gain of the emitter follower. (10 marks)
- (iii) Show that the output resistance of the emitter follower is given by

$$R_0 = \frac{r_\pi + R_S}{h_{fe} + 1}$$

where  $r_\pi$  represents the input resistance of the transistor  
 $R_S$  is the internal resistance of the voltage source and  
 $h_{fe}$  is the current gain of the transistor. (7 marks)

- (b) A common-collector amplifier has a load resistance of  $2.7 \text{ k}\Omega$ . The a.c. current gain and input resistance of the transistor in the amplifier are 200 and  $700 \Omega$ , respectively. The internal resistance of the voltage source is  $600 \Omega$ . Calculate the voltage gain and output resistance of the amplifier. (6 marks)

**QUESTION 5**

- (a) Use operational amplifiers to design circuits which correspond to the following ideal relationships between the output and input voltages.

(i)  $v_{out} = 500 \int v_{in(1)} dt + (3 \times 10^{-3}) \frac{dv_{in(2)}}{dt}$  (13 marks)

(ii)  $v_{out} = -10v_{in(1)} + 5v_{in(2)} - 20v_{in(3)}$  (8 marks)

Label the circuit diagrams you have designed, showing the values of the components used.

- (b) Suppose that you were required to build the op-amp circuit shown in Fig. 4, which gives a voltage gain of 100. What values of  $R_1$  and  $R_2$  would you need for this purpose?

(4 marks)

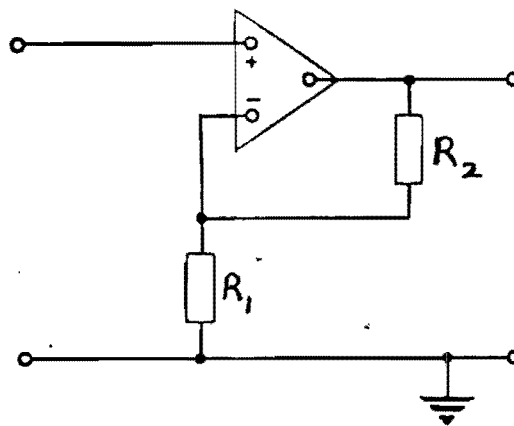


Fig. 4