

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE & ENGINEERING**

**DEPARTMENT OF PHYSICS**

**SUPPLEMENTARY EXAMINATION 2012/2013**

**TITLE OF PAPER : ELECTRONICS II**

**COURSE NUMBER : P312**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE  
SHOWN IN THE RIGHT-HAND MARGIN.**

**THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE  
INVIGILATOR.**

**QUESTION 1**

- (a) Explain how the input resistance of a device, such as an amplifier, can be measured. Use a schematic diagram and appropriate equations to illustrate your point. (5 marks)
- (b) Fig. 1 shows a low-pass filter circuit. The amplitude of the input voltage,  $v_i$  is 10 V.
- (i) Determine the cut-off frequency of this filter (in Hertz). (2 marks)
- (ii) Calculate the magnitudes of  $v_o$  when  $v_i$  has a frequency 500 Hz, 1 kHz, and 2 kHz. (7 marks)

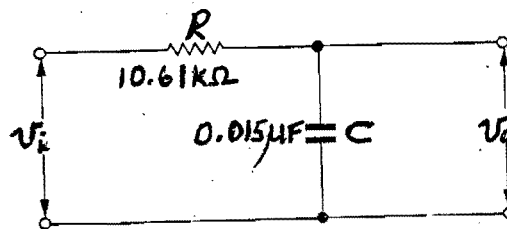


Fig. 1

- (c) (i) Calculate  $v_{out}$  as a function of time for the circuit shown in Fig. 2 when  $v_{in} = A \sin \omega t$ ,  $A = 500 \text{ mV}$  and  $\omega = 100 \text{ rad.s}^{-1}$ . (5 marks)
- (ii) Sketch and label graphs of  $v_{out}$  and  $v_{in}$  against time. Sketch them on the same axis. (6 marks)

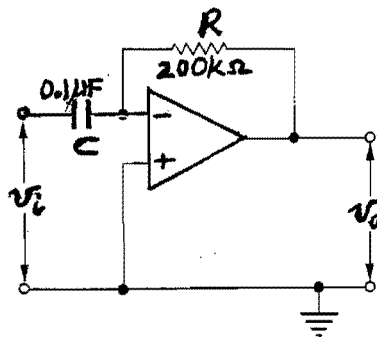


Fig. 2

## QUESTION 2

(a) Fig. 3 represents a free-running multivibrator.

- (i) Explain how this multivibrator works. Assume that the a.c. current gain of transistor  $T_1$  is higher than that of transistor  $T_2$ . (4 marks)
- (ii) With the aid of a table, sketch the waveforms observed at points P, Q, R and S. Label them. (12 marks)

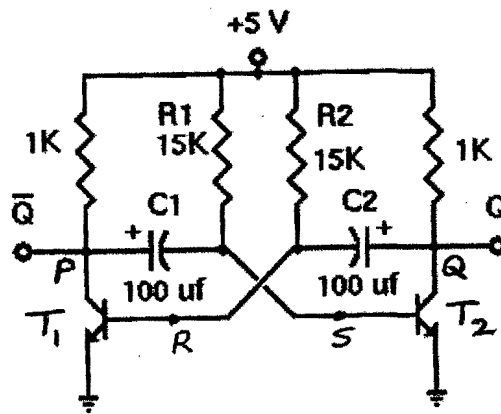


Fig. 3

- (b) (i) Write an expression for the frequency of oscillation of a phase shift oscillator which is made up of a BJT amplifier and an RC ladder network. The ladder network consists of equal resistors and equal capacitors. (2 marks)
- (ii) Consider each of the capacitors to be of capacitance  $C = 0.01 \mu\text{F}$  whilst each of the resistances of the resistors can be varied between  $2 \text{ k}\Omega$  and  $200 \text{ k}\Omega$ .  
Calculate the minimum and maximum frequencies which can be generated by the oscillator. (4 marks)
- (iii) Explain why the open-loop gain of the amplifier used in the phase shift oscillator must be of magnitude greater than or equal to 29. (3 marks)

### QUESTION 3

- (a) Consider the RLC bandpass filter shown in Fig. 4.
- (i) Derive an expression for the magnitude of the transfer function of this filter. (5 marks)
- (ii) Derive the expression for the resonant frequency. (4 marks)
- (iii) What is the value of the resonant frequency? (2 marks)
- (iv) Determine the Q-factor. (2 marks)
- (v) Calculate the cut-off frequencies,  $f_1$  and  $f_2$ . (6 marks)
- (vi) Calculate the bandwidth of the filter. (1 mark)

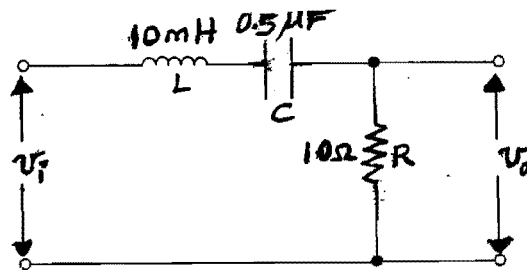


Fig. 4

- (b) Calculate the phase difference between  $v_o$  and  $v_i$  for the high-pass filter shown in Fig. 5, when  $v_i$  has a frequency of 20 kHz. (5 marks)

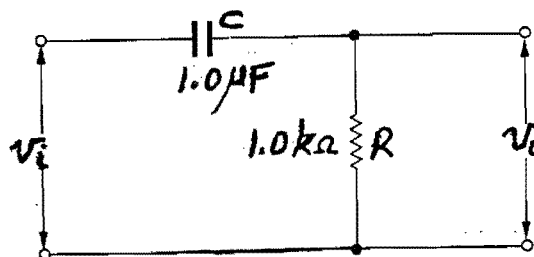


Fig. 5

#### **QUESTION 4**

- (a) (i) What is meant by degenerative feedback in amplifiers? (3 marks)
- (ii) Explain what is meant by the Barkhausen criterion? (3 marks)
- (b) State two distinct advantages of inverse feedback to an amplifier. (3 marks)
- (c) An amplifier has an open-loop gain of magnitude A. A fraction B of its output signal voltage is fed back to the input so as to reduce the signal at the input.  
Derive an expression for the gain with feedback. (5 marks)
- (d) An amplifier has the following properties:  
Open-loop gain =  $-500$   
Feedback is applied with a feedback factor of 0.2
- (i) What is the loop gain? (2 marks)
- (ii) Find the voltage gain with feedback. (2 marks)
- (iii) Determine the percentage fall in gain with feedback if the open-loop gain of the amplifier falls by 20 per cent. (7 marks)

**QUESTION 5**

(a) Fig. 6 shows an operational integrator.

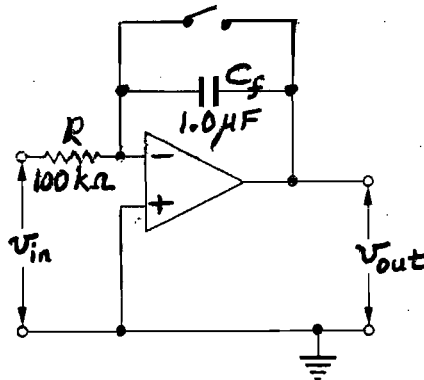


Fig. 6

- (i) Write down the relationship between  $v_{out}$  and  $v_{in}$  for a circuit shown in Fig. 6. (1 mark)
  - (ii) Calculate  $v_{out}$  as a function of time when  $v_{in} = -10$  mV. Sketch graphs of  $v_{out}$  and  $v_{in}$  with respect to time and label them. (5 marks)
  - (iii) Calculate  $v_{out}$  as a function of time when  $v_{in}$  is a voltage that varies sinusoidally with time. The voltage signal has an amplitude of 10 V and a frequency of 100 Hz. Sketch graphs of  $v_{out}$  and  $v_{in}$  as a function of time and label them (9 marks)
- (b) The equation below represents an ideal relationship between the output voltage,  $v_o$  and the input voltage,  $v_i$  of a circuit. Use operational amplifiers to design this circuit and label it.

$$v_o = -(v_i - 2 \times 10^{-4} \int v_i dt) \quad (10 \text{ marks})$$