

UNIVERSITY OF SWAZILAND

95

FACULTY OF SCIENCE AND ELECTRONIC ENGINEERING

DEPARTMENT OF PHYSICS

SUPPLEMENTARY EXAMINATION 2013/2014

TITLE OF PAPER : ELECTRONICS I

COURSE NUMBER : P311

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.

THIS PAPER HAS 7 PAGES, INCLUDING THIS PAGE.

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

QUESTION 1

96

- (a) Suppose that you were required to plot the drain and transfer characteristics of an n-channel JFET. Sketch the diagram of a circuit you would connect to measure these characteristics and label it. (3 marks)
- (b) Sketch and label typical drain and transfer characteristics of any n-channel JFET. (4 marks)
- (c) With the aid of the drain and/or transfer characteristics:
- explain why the JFET can be used as a voltage controlled resistor; (3 marks)
 - explain how you would determine the transconductance from the transfer characteristics. (4 marks)
- (d) When the gate-source voltage, V_{GS} of a JFET is kept constant, a change in the drain-source voltage of 2 V leads to a corresponding change in the drain current of 0.5 mA. Use this information to calculate the drain resistance, r_d of the JFET. (5 marks)
- (e) The circuit in Fig. 1 represents a common-source amplifier. The mutual conductance of the JFET is 10 mS.
- Calculate the voltage gain of the amplifier. (2 marks)
 - Calculate I_D and V_D , when $V_{GS} = -1.0$ V (4 marks)

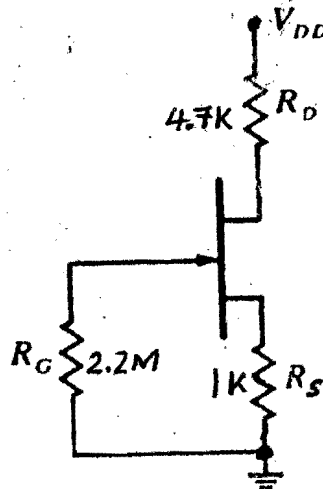


Fig. 1

QUESTION 2

- (a) Describe the operation of an npn transistor when it is connected in the forward-active mode. Use a suitable diagram for illustration. (10 marks)
- (b) The characteristics of a typical bipolar junction transistor (npn) are given in Fig. 2.
- (i) Draw the loadline on the enlarged characteristics shown on page 7, when the supply voltage, $V_{CC} = 8\text{ V}$ and the collector resistor, $R_C = 1\text{ k}\Omega$. (4 marks)
- (ii) Select a suitable quiescent point on one of the characteristics and estimate the quiescent values of I_B , I_C and V_{CE} . (3 marks)
- (c) Consider the circuit shown in Fig. 3. Calculate V_B , R_C and R_E using the following voltages and current:

$$V_{CE} = 9\text{ V}$$

$$V_E = 6\text{ V}$$

$$V_{BE} = 0.6\text{ V}$$

$$I_E = 3\text{ mA}$$

(8 marks)

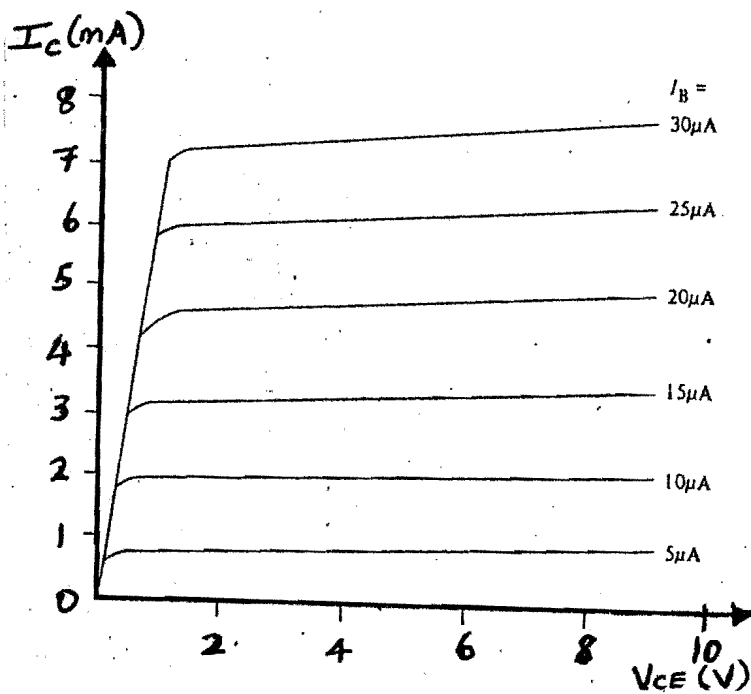


Fig. 2

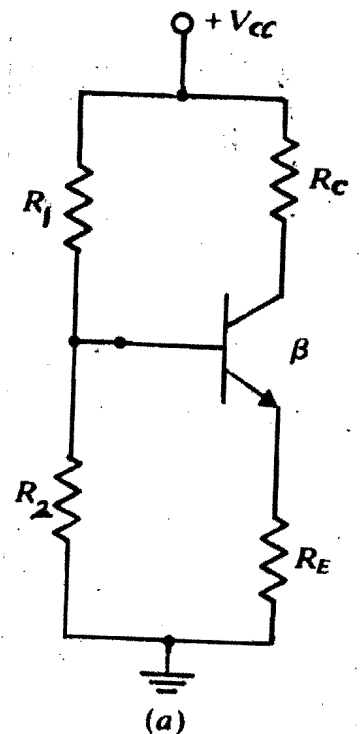


Fig. 3

QUESTION 3

98

- (a) A 0.1 mF capacitor is used to filter the output of a half-wave rectifier. The transformer secondary voltage has a frequency of 50 Hz and an amplitude of 56 V. The average current through the load is 20 mA. Calculate the following:
- (i) the peak value of the ripple voltage; (4 marks)
 - (ii) the average voltage across the load resistor, R_L . (2 marks)
- (b) A half-wave rectifier circuit consists of a diode and a load resistor R_L . It operates on an a.c. mains supply of 240 V_{rms}. The turns ratio of the step-down transformer is 0.25. Calculate the following:
- (i) the amplitude of the secondary voltage of the transformer; and (3 marks)
 - (ii) the average voltage across R_L . (2 marks)
- (c) A Zener diode with the specifications listed below is used in a voltage regulator circuit.

Knee current = 20 mA

Zener voltage = 9.1 V

Maximum power rating of the Zener diode = 1.3 W

The voltage at the input of the regulator circuit is 20 V \pm 10% and the load current, I_L = 30 mA.

- (i) Sketch the circuit diagram of the voltage regulator circuit and label it; (2 marks)
- (ii) Calculate the series resistance; (7 marks)
- (iii) Calculate the power dissipated in the diode when the supply voltage is 22 V. (5 marks)

QUESTION 4

96

- (a) Sketch the energy-band diagrams for the following materials. Label the diagrams and interpret the meaning of each diagram:
- (i) intrinsic silicon; (5 marks)
 - (ii) n-type silicon. (5 marks)
- (b) A silicon diode has a reverse saturation current of 10 nA when the junction temperature is 27 °C. The maximum current rating of this diode is 5 A.
- (i) Calculate the forward current and forward voltage when the incremental resistance of the diode, $r_d = 100 \Omega$. (7 marks)
 - (ii) If the diode is forward biased and the voltage across it is 0.5 V, what will be the forward current? (3 marks)
 - (iii) How high will the junction temperature be when the forward current is 5A and the forward voltage is 0.7 V? (5 marks)

QUESTION 5

140

- (a) Explain, briefly, how you would manufacture a p-channel junction field effect transistor. (7 marks)
- (b) With the aid of a diagram(s) and characteristics, discuss the principle of operation of the p-channel junction field effect transistor. (8 marks)
- (c) (i) Sketch the small signal equivalent circuit of a common-source amplifier. (3 marks)
- (ii) Use the equivalent circuit to show that the gain of the common-source amplifier, A_v is given by

$$A_v \propto \frac{r_d R_D}{r_d + R_D},$$

where r_d and R_D have their usual meanings. (4 marks)

- (d) The transistor used in a source follower circuit has a mutual conductance of 15 mS. The source resistor $R_S = 5 \text{ k}\Omega$. Calculate the voltage gain of the follower and its output resistance. (3 marks)

STUDENT'S EXAMINATION NUMBER:.....

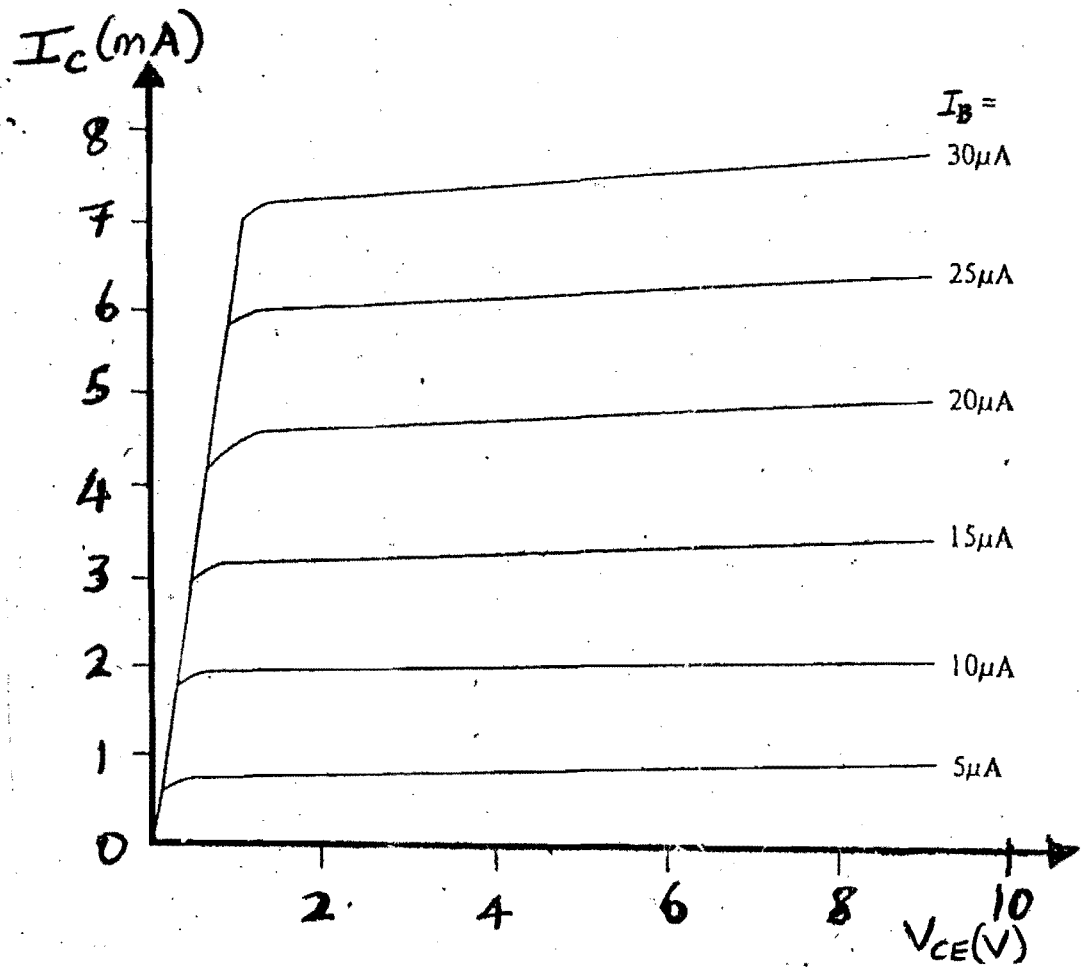


Fig. 2 (enlarged)