

**UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT OF PHYSICS**

MAIN EXAMINATION, MAY 2018

TITLE OF PAPER : ELECTRONICS II
COURSE NUMBER : PHY 312
TIME ALLOWED : THREE HOURS
INSTRUCTIONS : Answer FOUR (4) questions only.
: Each Question carries **25 Marks**
: Marks for different Sections are shown
in far Right margin.

THIS PAPER HAS 6 PAGES, INCLUDING THIS ONE.

**DO NOT OPEN THE PAPER UNTIL PERMISSION IS GRANTED BY
THE INVIGILATOR.**

1. (a) What is a band pass filter? [2]
 (b) Show that the transfer function of a series *RLC* band pass filter shown in Figure 1 may be written in the form

$$H(j\omega) = \frac{K}{1 + jQ \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)}$$

and identify the symbols in the expression. [8]

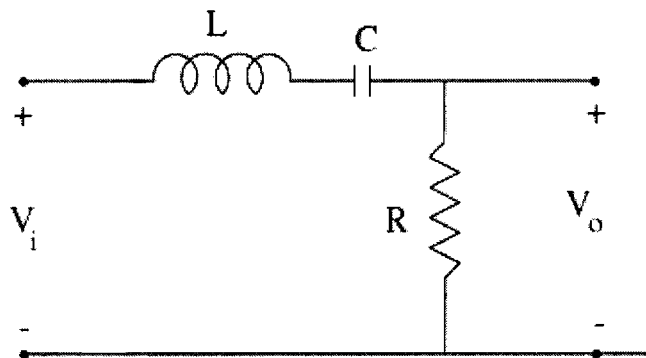


Figure 1: RLC band pass filter

- (c) Given a RLC band pass filter with a lower cutoff frequency of 1 kHz and a bandwidth of 3 kHz, determine the center frequency and Q of this circuit. [6]
 (d) Sketch the circuit diagram of a terminated *RC* low-pass filter and derive a general expression for the magnitude of its transfer function in terms the signal frequency f , and the cut-off frequency f_c . [9]

2. (a) In automated control systems, the output is usually optimized by a feedback mechanism. Distinguish between positive feedback and negative feedback. [2]
- (b) State six advantages of negative voltage feedback in amplifiers. [3]
- (c) Using a circuit diagram, derive an expression for the gain A_f of an amplifier with feedback in terms of the gain, A , of the amplifier without feedback and the feedback factor k . [6]

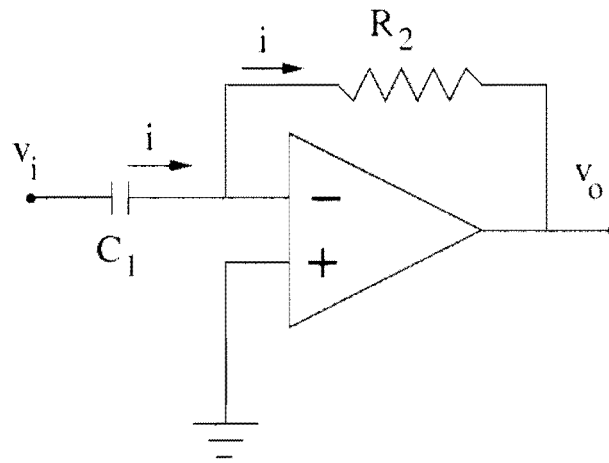


Figure 2: Differentiator Amplifier

- (d) Figure 2 shows the circuit of differentiator amplifier.
- i. Derive the expression for the output, V_{out} in terms of the input V_i , R_2 and C_1 . [4]
 - ii. Derive the expression for the voltage transfer function of the circuit, and mention the limitation of the amplifier. [4]
 - iii. How would you modify the above circuit to overcome the limitation mentioned in (d) ii? [3]
 - iv. Sketch $|H(j\omega)|$ with frequency and explain the behavior of the response function. [3]

3. (a) Draw the circuit diagram of an op-amp and label all the terminals. [2]
 (b) List the most important assumptions of an ideal op-amp and briefly explain the consequences of each in simplifying the op-amp equivalent circuit. [6]
 (c) Figure 3 shows a difference amplifier circuit.
 i. Show that [4]

$$V_o = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_2 - \frac{R_f}{R_1} V_1$$

- ii. If $R_1 = R_2 = R_3 = R_f$ and $V_1 = -1.0 V$ (dc) and $V_2 = 0.1 \sin \omega t$, sketch V_o for at least one cycle. [2]

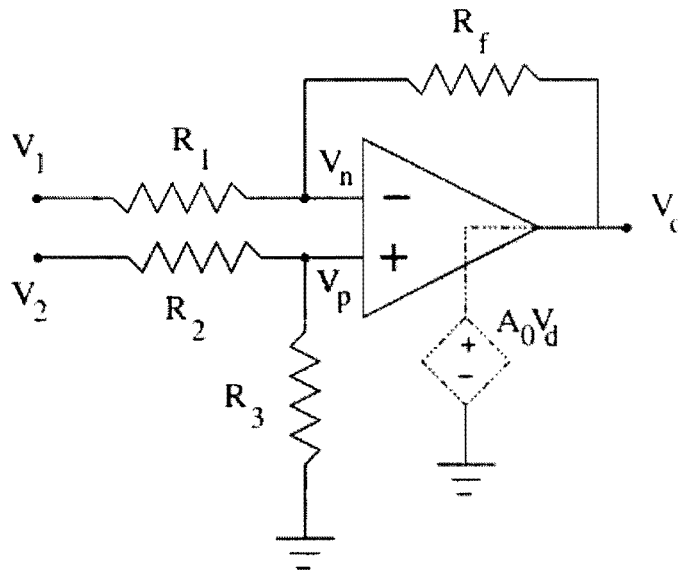


Figure 3: Difference amplifier

- (d) Use operational amplifiers and appropriate components to design a circuit that obeys the following relationship between the output voltage, v_o and the input voltage, v_i : [11]

$$v_o(t) = 3 \times 10^{-4} \frac{dv_i}{dt} + 10 \int v_i dt$$

4. (a) State the Barkhausen condition necessary for oscillation to occur. [2]
- (b) A 3-stage RC Phase Shift Oscillator is required to produce an oscillation frequency of 6.5kHz. If 1nF capacitors are used in the feedback circuit,
- i. calculate the value of the frequency determining resistors. [2]
 - ii. calculate the value of the feedback resistor required to sustain the oscillations. [2]
 - iii. draw the circuit diagram of the above oscillator. [2]
- (c) i. Sketch a labeled circuit diagram of a Wien-Bridge Oscillator which utilizes a two-stage amplifier [3]
- ii. Describe the principle of operation of the Wien-Bridge oscillator. [12]
 - iii. Calculate the frequency of oscillation of this oscillator when $R = 10 \text{ k}\Omega$ and $C = 0.01 \mu\text{F}$. [2]

5. (a) Sketch the circuit diagram of a physical (not an ideal) operational integrator and label it. [2]
- (b) i. The input voltage of the operational integrator is $v_{in} = 0.5 \sin 100t$. The capacitance of the feedback capacitor, $C_f = 1.0 \mu\text{F}$ while the external resistance at the input of the integrator, $R_{in} = 100 \text{ k}\Omega$. Find the expression for v_{out} as a function of time for the integrator. [7]
- ii. Sketch graphs of v_{in} and v_{out} as a function of time on the same axes. Label both axes. [3]
- (c) Define the following concepts as they pertain to amplifiers
- i. Bandwidth [1]
- ii. Slew rate [2]
- (d) The circuit diagram in Figure 4 is a voltage-to-current converter with $I_L = gV_i$. Find the value of g and show that it is independent of R_L . (Assume OpAmp is ideal). [10]

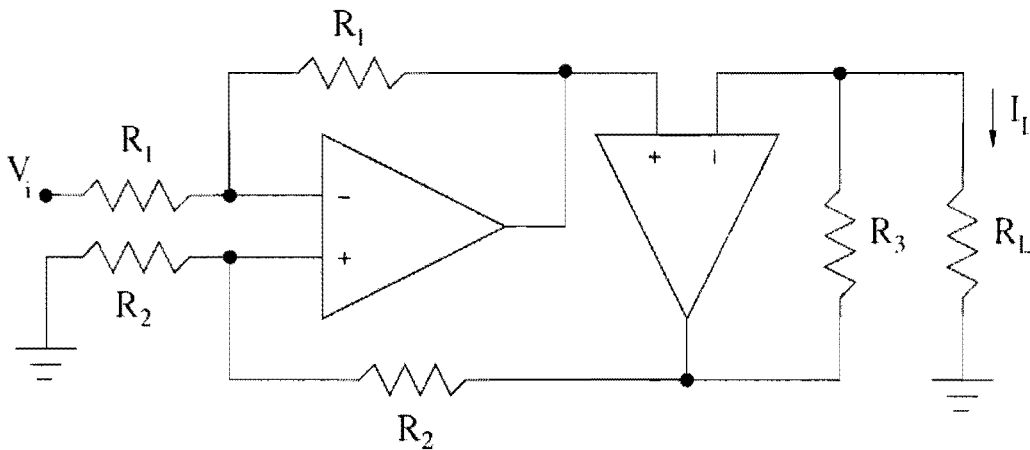


Figure 4: Voltage-to-Current Converter

END