

UNIVERSITY OF SWAZILAND  
FACULTY OF SCIENCE AND ENGINEERING  
DEPARTMENT OF PHYSICS

MAIN EXAMINATION, DECEMBER 2019

TITLE OF PAPER : ELECTRONICS 1

COURSE NUMBER : PHY 311

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : Answer **FOUR** (4) questions only.

: Each question carries **25 Marks**

: Marks for different sections are shown  
in far right margin.

THIS PAPER HAS 6 PAGES, INCLUDING THIS ONE.

DO NOT OPEN THE PAPER UNTIL PERMISSION IS GRANTED BY  
THE INVIGILATOR.

1. (a) Define the following
- (i) Intrinsic semiconductor [1]
  - (ii) Doping [1]
  - (iii) pn-junction. [1]
- (b) Sketch a bridge rectifier and the output (without a smoothing capacitor) and explain how it works. [5]
- (c) Assume that a smoothing capacitor  $C$  was connected across the load resistor of the bridge rectifier. With the aid of a schematic diagram of the variation of the output signal with time, show that the ripple voltage,  $V_r$  can be written as [7]

$$V_r = \frac{I_{av}}{2fC},$$

where  $I_{av}$  is the d.c. current and  $f$  is the frequency.

- (d) Modify the bridge circuit in (b) above to obtain a voltage doubler circuit and sketch the output signal if the input is sinusoidal. [4]
- (e) Consider the circuit in Figure 1 .
- (i) Using the Zener diode model, obtain the load line equation for the circuit. [4]
  - (ii) Sketch the I-V characteristics of the diode together with the load line. [2]

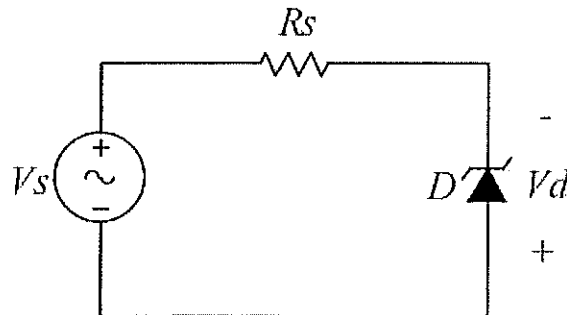


Figure 1

2. (a) Sketch and label typical drain and transfer characteristics of an n-channel JFET. [4]
- (b) Write the equation for JFET transfer characteristic curve. [2]
- (c) When the gate-source voltage,  $V_{GS}$  of a JFET is kept constant, a change in the drain-source voltage of 2 V leads to a corresponding change in the drain current of 0.5 mA. Use this information to calculate the drain resistance,  $r_d$  of the JFET. [5]
- (d) The circuit in Fig. 2 represents a common-source amplifier. Assume  $I_{DSS} = 770 \mu A$  and  $V_{GS(off)} = -3 V$ .

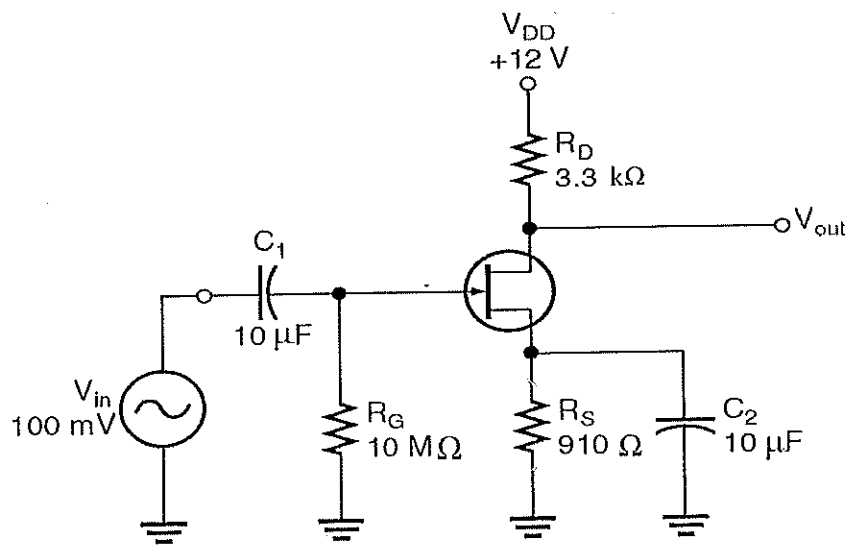


Figure 2: Common Source Amplifier

Calculate the following;

- i. the drain current,  $I_D$  [5]
- ii. the drain voltage  $V_D$  [2]
- iii. the transconductance,  $g_m$  [4]
- iv. the total output voltage of the amplifier. [3]

3. (a) With the aid of a circuit diagram, explain how a full-wave rectifier that utilises a center-tap transformer works. Sketch the output of the rectifier with reference to the transformer secondary voltage. [9]
- (b) A bridge rectifier with a smoothing capacitor operates from 60 Hz. A load resistance of  $1\text{ k}\Omega$  is connected across the output terminals. The peak value of the output voltage is 24 V and the ripple voltage is 4 V.
- (i) Sketch a graph of the output voltage against time with reference to the secondary voltage and label both axes. [4]
- (ii) Determine the capacitance of the capacitor. [6]
- (c) Fig.3 shows a half-wave rectifier with a smoothing capacitor. The average current through the load resistance is 10 mA. A period of oscillation of the secondary voltage is 20 ms and amplitude is 50 V. Calculate the average voltage across the load resistor. [6]

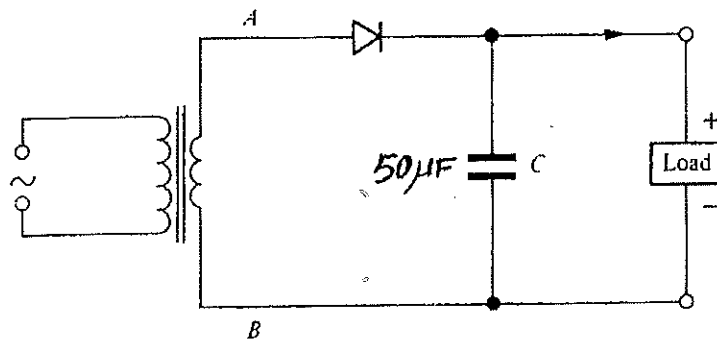


Figure 3

4. (a) Determine the Q-point for the circuit below and find the maximum peak value of base current for linear operation. Assume  $\beta_{DC} = 200$ . [7]

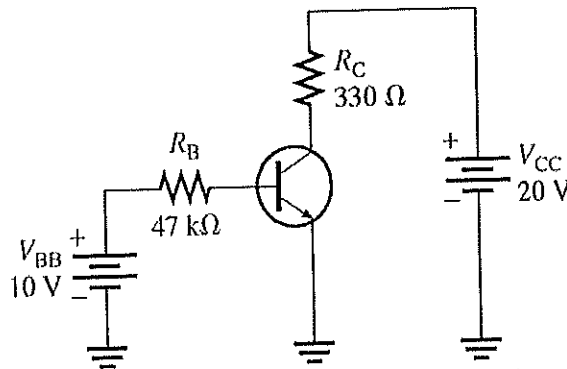


Figure 4: Base-bias

- (b) Consider the common-emitter amplifier shown in Figure 5,

(i) perform the dc analysis of the circuit. [5]

(ii) perform ac analysis of the circuit. [10]

(iii) Draw the waveforms. [3]

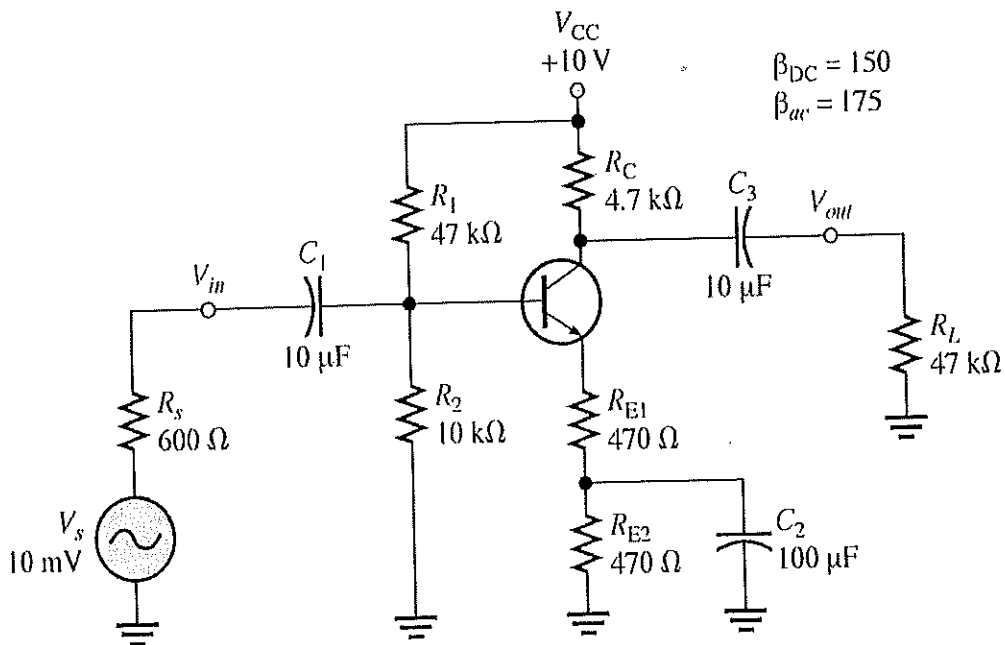


Figure 5: CE-Amplifier with  $R_L$

5. (a) Define the hybrid parameters of the transistor in terms of the d.c. currents and voltages . [2]
- (b) Describe how you would determine the hybrid parameters of a bipolar transistor from the input and output characteristics of the transistor. [6]
- (c) With reference to the circuit diagram in Fig.6, calculate the values of the dc voltages  $V_B$ ,  $V_C$  and  $V_{CE}$  and the direct currents  $I_B$  and  $I_E$ . Assume that the current  $I_{BB}$  flowing into the potential divider ( $R_1$  and  $R_2$ ) is much greater than  $I_B$  and  $V_{BE} = 0.6$  V and  $h_{FE} = 200$ . [15]

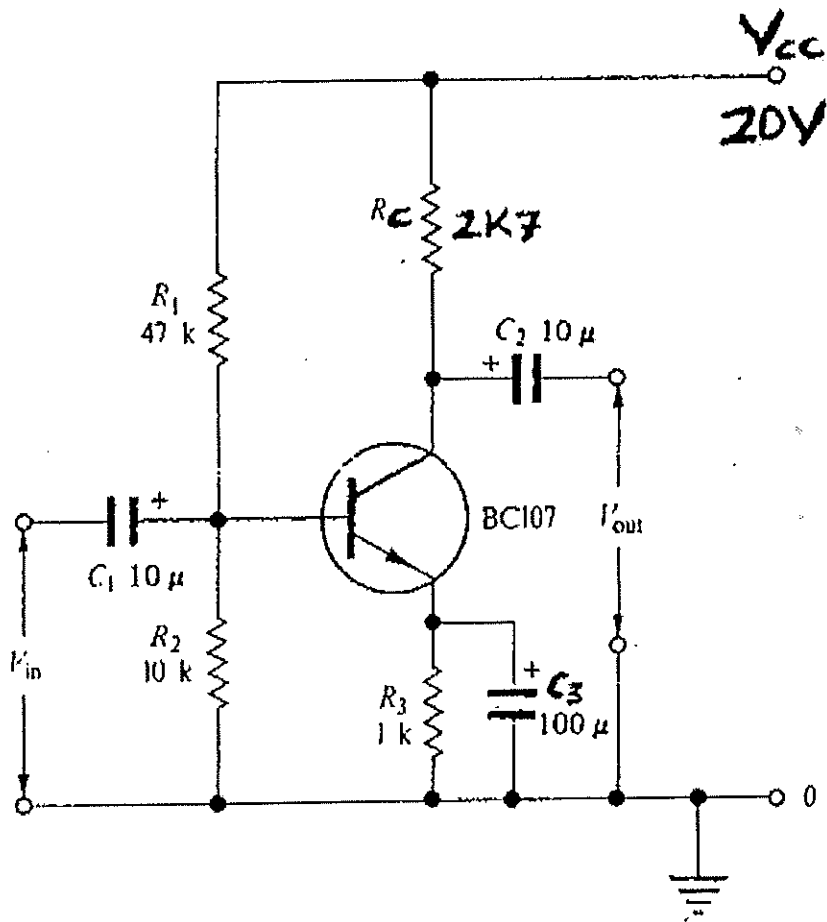


Figure 6

- (d) (c) State the relation between pinch-off voltage,  $V_P$ , and cutoff voltage,  $V_{GS(off)}$ . [2]